

A look on characterization of semiconductor devices

Tommy Rosenbaum (IFAG DES CDF AMS IMV TTN)
26.10.2021



Motivation + Goal

- › How do we need to characterize devices to describe them fully and hence, (at best) be able to simulate them correctly?
 - I do not want to talk about modeling here
 - i.e. whether we can match the characterization data with a compact model is not relevant for this question

- ⇒ What kind of analyses do we need to fully describe device behavior?
 - TRAN+DC+AC+HB+XXX?!

How to crack a nut?

- › The hammer



- › The nutcracker




- › As a generic tool, I'd guess the hammer wins, but in this example...
- › If you have the choice, you would use the nutcracker, right?
 - I'll use this reference later during the presentation


The whole world runs in transient

- > Keep in mind that every signal $V_{\text{sig}}(\mathbf{t})$ in the real world runs in transient
 - Strictly speaking, there is no DC, AC, ...
 - All other analyses are (e.g. mathematical) ways to describe what is going on in transient
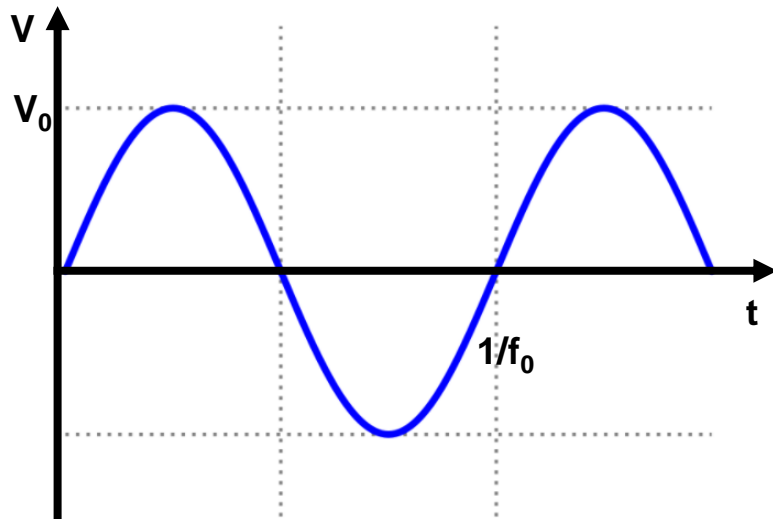
> Example: Sine wave $V_{\text{sin}} = V_0 \cdot \sin(t \cdot f_0 \cdot (2 \cdot \pi))$



.FOUR

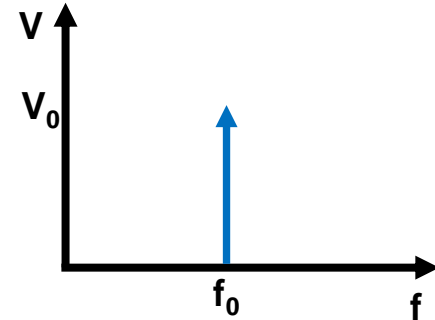

- > The sine wave can be broken down to two numbers (V_0, f_0)
- > .FOUR is the nutcracker for sine waves

Let us break down the transient world

- › $V_{\text{sig}}(\mathbf{t}) = \text{const}$ (for $t > t_{\text{settle}}$)
 - Well, this is obviously a .DC/(.OP)
 - Somehow, this is what is done when a RAMP is used for finding a DC solution using a transient
- › $V_{\text{sig}}(\mathbf{t}) = \text{const} + V_0 \cdot \sin(t \cdot f_0 \cdot (2 \cdot \pi))$ (for $t > t_{\text{settle}}$ and sufficiently small V_0)
 - .DC/(.OP) + .AC
 - All capacitors + inductors (and whatever weird charge/flux controlled elements you have within compact models) simplify to frequency dependent resistors/capacitors/inductors (and as our frequency is const, ...)
 - ⇒ We are somehow back to running another .DC on top of our original .DC
- › I can recommend the lecture notes from Prof. W. Schwarz (F. Kurz wrote it down)
 - R.I.P.
 - <http://fkurz.net/et/>


Let us break down the transient world

- › Arbitrary $V_{\text{sig}}(\mathbf{t})$
 - Well, this might not be easy ...

- › Without dynamic contributions
 - Then all voltages+currents in the circuit will instantly follow the stimulus
 - ... and we essentially have a single .DC analysis for each timepoint

- › With dynamic contributions
 - From one timepoint to the next
 - ... for capacitors

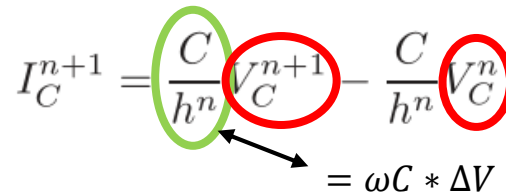
$$I_C^{n+1} = \frac{C}{h^n} V_C^{n+1} - \frac{C}{h^n} V_C^n \quad (\text{backward Euler})$$



[1]: QUCS technical papers
Stefan Jahn, et al., 2007

- ... for inductors
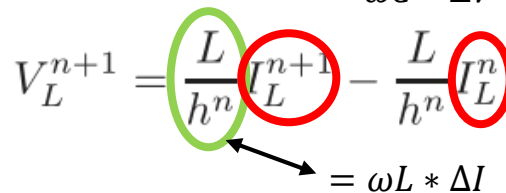
$$V_L^{n+1} = \frac{L}{h^n} I_L^{n+1} - \frac{L}{h^n} I_L^n$$




Let us break down the transient world

- › Arbitrary $V_{\text{sig}}(t)$
 - It seems that with dynamic components, a transient gets additional contributions that can also be described by an .AC

- › Another way to phrase it
 - A .DC bias describes how a bias behaves
 - An .AC tells us how the device can exit the current bias and enter a new one


A transient example

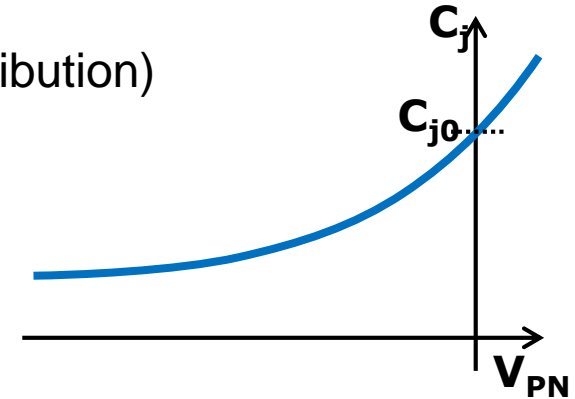- > Simple diode
 - Consisting of a diode equation (for a static contribution)
 - $I_{dio} = I_s [\exp(V_j/V_{th}) - 1]$
 - ... and junction capacitance (for a dynamic contribution)





- > Apply a voltage pulse to the diode
 - Note that we will apply a negative pulse over the diode

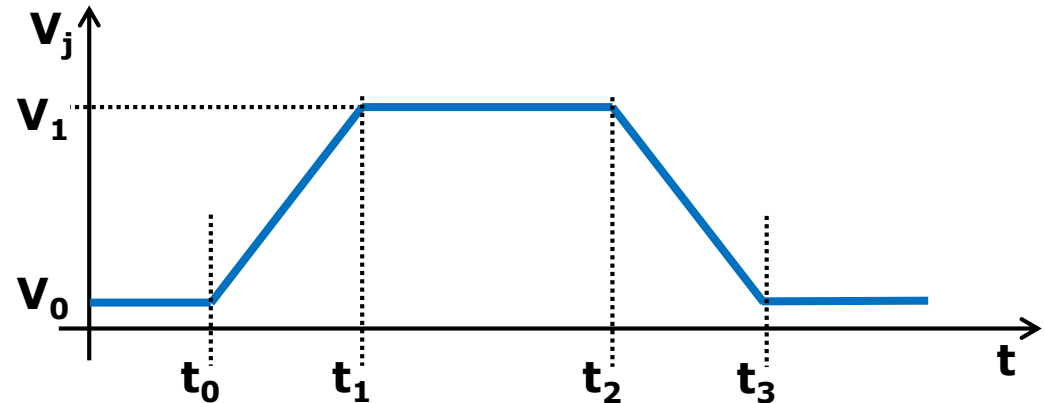⇒ We bias the diode in forward at first and the first pulse will turn it off




Let us run a true .TRAN simulation first

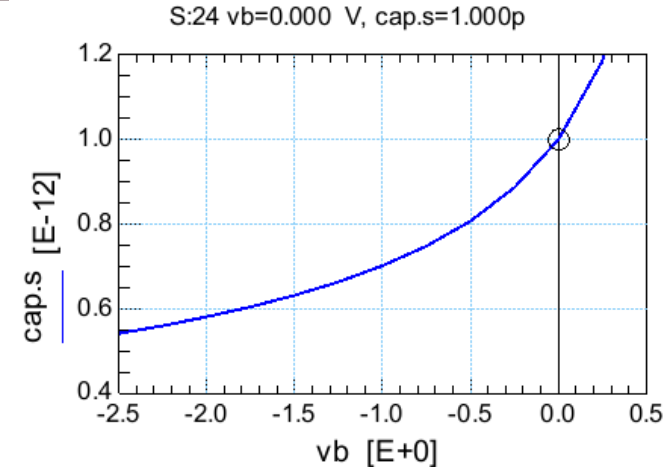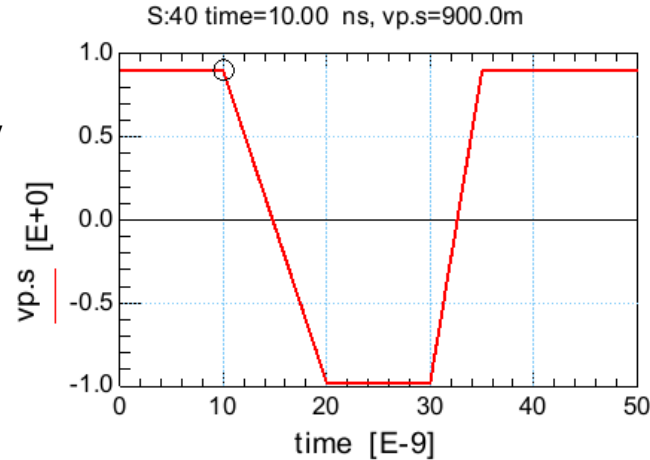- > The example
 - $V_0 = 0.9V$, $V_1 = -1V$
 - $t_1 - t_0 = 10ns$
 - $t_2 - t_1 = 5ns$



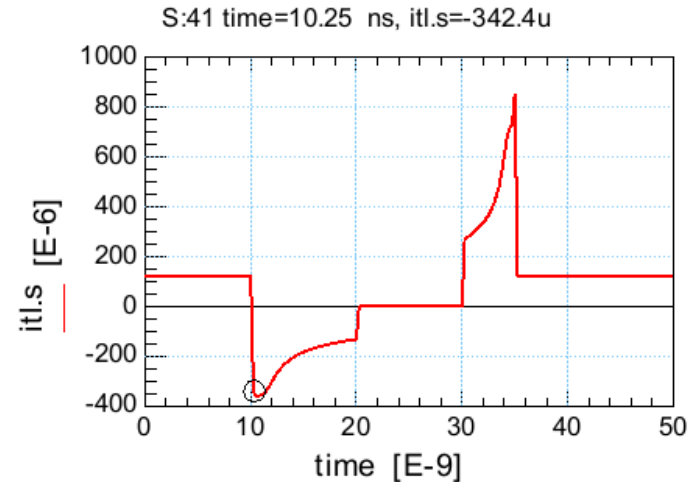
- > The result is rather simple 😊
 - Let us interpret it a bit ...



Let us describe the transient simulation with DC+AC

- › Discretize the voltage pulse in e.g. 250ps wide steps
 1. Run a DC at the current timepoint
 - At the initial timepoint (t=0) we assume no dynamic contributions
 2. Run an AC at $\omega = 1/250ps = 4GHz$ at the current DC bias
 - Determine the effective resistance of all dynamic elements
 - e.g. $R_{eff} = 1/(\omega C)$
 3. Replace all dynamic elements by a surrogate circuit
 - For a capacitor: effective resistance in series with voltage source (V_C^n)
 4. Go back to 1 and repeat for the next timepoint
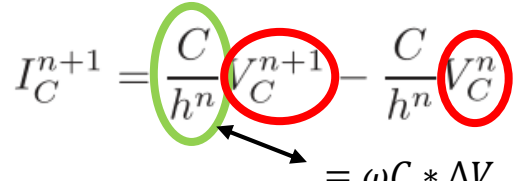
$$I_C^{n+1} = \frac{C}{h^n} V_C^{n+1} - \frac{C}{h^n} V_C^n \quad (\text{backward Euler})$$




 $= \omega C * \Delta V$

Let us describe the transient simulation with DC+AC

› Result

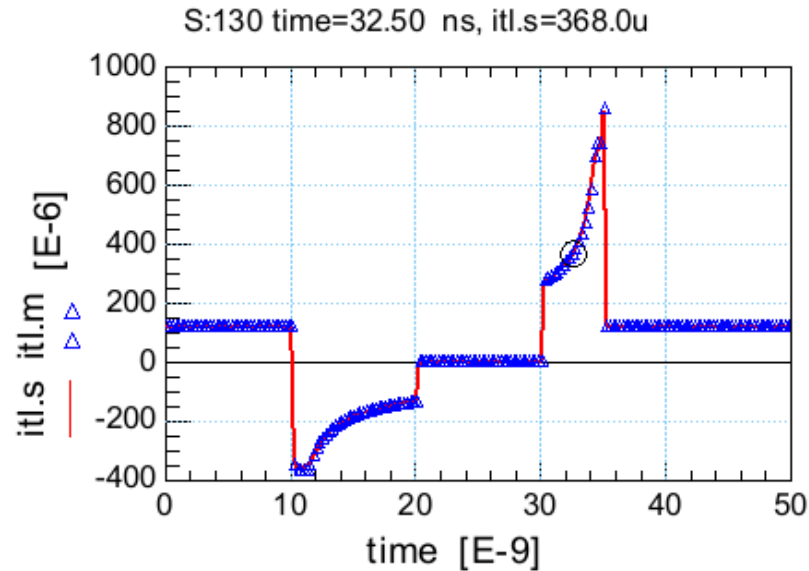- Lines correspond to a true .TRAN simulation
- Markers correspond to the .DC/.AC approach



⇒ We have a match 😊

Conclusion

1. The inverse transient time step may be considered as an effective frequency
 2. .DC and .AC seem to be sufficient to describe transient behavior
- › Are there limitations?
 - › Do we need .HB or other RF analyses?
 - At least for characterization normally we do not
 - Why? Nonlinearities come from bias dependence of conductances/capacitances (which we have determined from .AC at different bias)
 - Well, you may enter a different static bias, which you do not reach with normal DC
 - And you also stress your device differently (as it is a dynamic stress)
3. If you characterize a device in all bias points with .DC and .AC at all frequencies you collected all data to fully describe it
- › Do not get me wrong
 - I am not saying that other analyses are useless
 - Analyses need to be chosen according to application for true verification
 - Do not use DC+AC to check a transient FoM (=figure of merit). Use the nutcracker!

How characterization is done in practice?

- › I hope everybody does DC and AC ...



Part of your life. Part of tomorrow.