

Remarks on RF and Breakdown Modeling of Integrated Diodes

AKB 2023, Corbeil-Essonnes, France

Kund Molnár
10.11.2023


Agenda

1. Level-1 RF Extractions with 1 Internal Node.
2. Level-1 RF Extractions with 2 Internal Nodes.
3. Diode_CMC Shortcoming in RF Modeling.
4. Soft Breakdown Modeling Options.
5. Conclusions




Diode RF Extractions: S-Parameter Setup

Diode RF Modeling

S_{11}

 


S_{21}

  
 


Diode RF Extractions: Cp-Gp from Admittance

Diode RF Modeling

 


Diode Level-1

  


Adjusting R_s seems to be a good solution...

C_D - Freq

 


C_D - V_c

 



$$C_D = \frac{\text{Im}(Y)}{\omega}$$

Diode RF Extractions: Cs-Rs from Impedance

Diode RF Modeling

 


Diode Level-1

  


Not sufficient to reproduce the frequency dependence.

C_D - Freq

 




C_D - Vc

 



$$C_D = - \frac{1}{\omega \cdot \text{Im}(Z)}$$

Diode RF Extractions: Cs-Rs from Impedance with 2 Internal Nodes

Diode RF Modeling

 
 
 


  2 internal nodes are needed to produce this behavior!





Diode RF Extractions: Cp-Gp from Admittance with 2 Internal Nodes

Diode RF Modeling

   


Can be produced by simple $R_s - C_s$ equivalent circuit too.
  
$$G_p = \frac{\omega^2 C_s^2 R_s}{1 + (\omega C_s R_s)^2}$$



Diode_CMC Shortcoming

Diode RF Modeling

 


Resistance: one component with 4 possible scaling rules:

Area (R_{SBOT}), Gate-edge (R_{SGAT}), Perimeter (R_{SSTI}) and fixed (R_{COM})

$$R_{S_{nom}} = \frac{1}{\frac{AB}{R_{SBOT}} + \frac{LG}{R_{SGAT}} + \frac{LS}{R_{SSTI}}} + R_{COM}$$

Capacitance: fully compatible with Level-1

 - Single branch implementation with one internal node.
- Not suggestiv of RF modeling.
- Subcircuit of 2 Diode_CMC diodes needed.





Unused components are to be eliminated:

1. Setting R_{COM1} & R_{COM2} (unscaled), $R_{sbot}=R_{ssti}=R_{sgat}=0$
2. Setting R_{SBOT1} & AB_1 and R_{SSTI2} & LS_2 , $R_{COM1}=R_{COM2}=0$, $R_{SBOT2}=R_{SSTI1}=R_{SGAT}=1e9$

Diode Soft Breakdown I

Diode Breakdown Modeling

  

Level1:





- Trap-assisted tunneling current used for modeling the soft breakdown region:
 - JTUN, JTUNSW (tunneling saturation currents)
 - NTUN (emission coeff., set to a large value e.g. $ntun > 10$)
- Hard breakdown: BV, NZ=1
- Area/Perimeter components (JS, JSW, CJO, CJSW etc) as usual.

Diode Soft Breakdown II

Diode Breakdown Modeling

Diode Subcircuit:

    - Composed of two Level1 diodes in parallel with series resistance.
- D_{FWD} : Forward and reverse DC including soft breakdown.
- D_{FWD} : Soft breakdown modeling using IBV, BV and NZ (slope).
- D_{BD} : Hard breakdown only, JS=JSW=CJ0=CJSW=0.
- D_{BD} : Resistance after BD can be adjusted with R_{BD} (fwd bias is not affected).



T=25, 80, 125 C

Conclusions

Diode RF & Breakdown Modeling

- Level-1: Cs-Rs extractions from impedance indicates best whether both internal nodes need to be activated.
- Diode_CMC: Should be extended to 2 internal nodes to make it more suitable for RF modeling.
- Two different approaches have been discussed with Level-1 for modeling complex BD behavior:
 - Utilizing the trap-assisted tunneling current.
 - Sharing the BD effect between two diodes. No advanced effects are needed. Resistance after BD.

Sensing is life

ami OSRAM

Thank you